



[4658] – 63

Seat No.	
----------	--

T. E. (Electrical) (Semester – I) Examination, 2014
POWER ELECTRONICS
(2008 Pattern)

Time : 3 Hours

Max. Marks : 100

- Instructions :** 1) Answers to the **two** Sections should be written in **separate** answer books.
2) Answer **any three** questions from **each** Section.
3) Black figures to the **right** indicate **full** marks.
4) **Neat** diagrams must be drawn **wherever** necessary.
5) **Use** of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is **allowed**.
6) Assume suitable data **if** necessary.

SECTION – I

1. a) Draw gate drive circuit for GTO. Discuss switching characteristics and give comparison between SCR and GTO. 8
b) Explain and compare R and RC firing circuit for SCR. 8
OR
2. a) Draw gate characteristics of SCR. Explain how value of gate voltage and gate current can be selected. 8
b) Why SCR is called as current controlled device ? Define Latching current and Holding current. 8
3. a) What are converters ? Explain with circuit diagram and waveforms working of 3 ϕ half controlled converter with highly inductive load. Deduce the equation for o/p voltage. Plot W/Fs at $\alpha = 60^\circ$. 10
b) Explain single phase dual converter. Draw waveforms for output voltage at $\alpha = 60^\circ$ and $\alpha = 150^\circ$. Comment on mode of operation of 1 ϕ dual converter at 60° and 150° . 8
OR
4. a) With neat circuit diagram and all necessary waveforms explain the working of three phase fully controlled bridge converter feeding RLE load. Explain modes of operation. 10
b) Write a note on selection of transformers and semiconductor devices for converters. 8
5. a) Describe the working of a two stage sequence control of voltage controllers for R load. What is the advantage of this controller over 1 ϕ full wave voltage controller ? 8
b) Discuss various technique adopted for protection of TRIAC and DIAC. 8

OR

P.T.O.



6. a) Explain static on load tap changing of transformer using a. c. regulators. Draw output voltage waveform using two stages. 8
- b) Explain four mode operation of TRIAC. 8

SECTION – II

7. A) Describe the switching characteristic of Power MOSFET and give applications with control requirements. 8
- B) Give a comparison between MOSFET and IGBT. 8

OR

8. A) Describe the basic structure of MCT. Give its equivalent circuit and explain the turn on and turn off process. 8
- B) Explain output and transfer characteristics of IGBT. 8
9. A) Explain four quadrant chopper feeding RLE load in detail. 8
- B) What is time ratio control in dc choppers ? Explain the use of TRC for controlling the output voltage in choppers. 8

OR

10. A) Explain the principle of operation of step up chopper. Derive expression for output voltage. 8
- B) Draw a power circuit diagram for a type-A chopper. Show load voltage waveforms for $\alpha = 0.3$ and $\alpha = 0.8$. For both these duty cycles, calculate : the average and rms values of output voltage in terms of source voltage. 8
11. A) What is a need for controlling the voltage at the output terminals of an inverter ? Describe and compare various methods employed for the control of output voltage of inverter. 9
- B) What is pulse width modulation ? Explain any one PWM technique in detail. 9

OR

12. A) Explain with circuit diagram and waveforms operation of single phase current source inverter. 8
- B) Explain working of three phase six step voltage source inverter in 180° mode of operation. For star connected load draw output voltage waveforms. Show devices conducting in each step. 10