### 

# [4656] - 103

Seat No.

#### F.E. (Semester – I) Examination, 2014 BASIC ELECTRONICS ENGINEERING (2012 Pattern)

Time : 2 Hours


Max. Marks : 50

Instructions : 1) Neat diagrams must be drawn wherever necessary.

- 2) Black figures to the **right** indicate **full** marks.
- *3)* Use of logarithmic tables slide rule, Mollier charts, electronic pocket calculator and steam table is **allowed**.
- 4) Assume suitable data, if **necessary**.
- 1. A) Compare performance of half wave rectifier and full wave rectifier with respect to following parameters :
  - 1) IDC
  - 2) Irms
  - 3) Rectifier efficiency
  - 4) Ripple factor
  - 5) PIV
  - 6) TUF.
  - B) Explain how transistor can be used as an amplifier with the help of D.C. load line approach.

OR

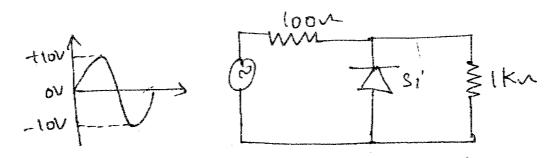- 2. A) Explain the operation of n-channel enhancement type MOSFET with its characteristics. 6
  - B) Determine the O/P waveform for the circuit shown in fig.



6

6

6

### [4656] – 103

## 

3.	A)	Explain the working of inverting summing amplifier with two inputs along with its wave forms.	6
	B)	State and prove the De-Morgan's theorem. Simplify the following Boolean expression :	
		$\overline{\overline{A}B} + A\overline{\overline{B}}$	6
		OR	
4.	A)	With the help of block diagram of IC555 explain its operation in Astable mode.	6
	B)	Compare Microprocessor and microcontroller.	6
5.	A)	Explain the operation of SCR with the help of V-I characteristics.	7
	B)	Explain the selection criteria of a Transducer.	6
		OR	
6.	A)	Define 'Dark current'. Draw and explain the characteristics of photo transistor.	6
	B)	Explain the construction of DIAC and draw its characteristics.	7
7.	A)	Draw and explain the electromagnetic or IEEE frequency spectrum.	7
	B)	Compare AM and FM.	6
		OR	
8.	A)	Draw and explain the block diagram of GSM.	7
	B)	A carrier of 10 V peak and frequency 100 KHz is amplitude modulated by a sinewave of 4 V peak and frequency 1000 Hz. Determine the modulation index for the modulated wave and draw the frequency spectrum for AM wave.	6

B/II/14/