

Nov-Dec-2009

Total No. of Questions—12]

[Total No. of Printed Pages—4

[3662]-203

S.E. (Comp. Engg.) (I Sem.) (Common to IT)

EXAMINATION, 2009

DIGITAL ELECTRONICS AND LOGIC DESIGN

(2008 COURSE)

Time : Three Hours

Maximum Marks : 100

N.B. :— (i) Answer questions 1 or 2, 3 or 4, 5 or 6 from Section I and questions 7 or 8, 9 or 10, 11 or 12 from Section II.

(ii) Answers to the two Sections should be written in separate answer-books.

(iii) Neat diagrams must be drawn wherever necessary.

(iv) Figures to the right indicate full marks.

(v) Assume suitable data, if necessary.

SECTION I

1. (a) What will be the Excess-3 code of any given 4-bit grey code number ? Show the truth table. [6]

(b) Express the following numbers in binary. Show your step by step equations and calculations : [6]

(i) $(1010.11)_{\text{Decimal}}$

(ii) $(428.10)_{\text{Decimal}}$

(c) Perform the following Hexadecimal subtraction and show your answer in Hexadecimal only : [6]

(i) $(387)_{\text{Hex}} - (2AC)_{\text{Hex}}$

(ii) $(587)_{\text{Hex}} - (4EB)_{\text{Hex}}$

P.T.O.

Or

2. (a) What is the max. equivalent decimal number represented by its max. equivalent 4-digit Hex number ? Also convert the following Hex numbers to get its equivalent octal and decimal : [8]

(i) $(ABC)_{Hex}$

(ii) $(DEF)_{Hex}$

- (b) What is De Morgan's theorem ? Solve the following using minimization technique : [10]

(i) $z = f(A, B, C, D) = \Sigma(0, 2, 4, 7, 11, 13, 15)$

(ii) $z = f(A, B, C, D) = \pi(1, 2, 3, 6, 8, 11, 14, 15).$

3. (a) With the help of Quine-McClusky technique determine the PI for the following equation : [10]

$$z = f(A, B, C, D) = \Sigma(0, 1, 3, 4, 6, 8, 10, 12, 14).$$

- (b) Explain standard TTL characteristics in brief. [6]

Or

4. (a) Draw 2-i/p standard TTL NAND gate circuit and explain operation of transistor (ON/OFF) with suitable conditions and truth table. [10]

- (b) Compare TTL and CMOS logic family. Also draw CMOS-NOR gate. [6]

5. (a) Draw and explain 4-bit BCD subtractor using IC 7483. Explain subtraction for $(9 - 5)_{BCD}$ and $(4 - 7)_{BCD}$. [10]

- (b) Explain the working of magnitude comparator using IC 7485. Choose suitable inputs. [6]

Or

6. (a) Design 12 : 1 mux using 4 : 1 multiplexers (with enable inputs).
Explain the truth table of your circuit in short. [8]
- (b) Explain DEMux (1 : 8) as a full adder and full subtractor. Show your design. [8]

SECTION II

7. (a) Explain the difference between combinational and sequential circuit. Also convert J-K flip-flop into D-FF and T-FF. Show the truth table. [8]
- (b) Draw 3-bit Asynchronous counter. Explain timing diagram for the same. [8]

Or

8. (a) What is MOD counter ? Explain MOD-27 counter using IC 7490. Draw design for the same. [8]
- (b) Explain Johnson counter with design for initial state '0110'. From initial state explain and draw all possible states. [8]
9. (a) What is ASM chart ? Design ASM chart for 3-bit up-down counter. [8]
- (b) What is VHDL ? Explain entity-architecture declaration for 2-bit X-NOR gate. [8]

Or

10. A sequential ring counter with present state '0001'. The circuit also have an input 'X'. If $X = 0$, then circuit will show next output else for $X = 1$ it will show initial state '0001'. Draw an ASM chart and state table for this circuit to generate the output using mux controller method. [16]

11. (a) Explain basic architecture of FPGA. [8]
(b) Explain basic microprocessor architecture. [8]

Or

12. (a) Explain the design model of PLA. [8]
(b) Explain in brief the working of Address bus, Data bus and Control bus by assuming a basic operation. [8]