

Total No of Questions: [8]		SEAT NO. : <div></div>	
[Total No. of Pages : 1 ]			
S.E. 2012 (INFORMATION TECHNOLOGY)			
DIGITAL ELECTRONICS & LOGIC DESIGN (214443)			
(Semester - I)			
Time: 2 Hours		Max. Marks : 50	
Instructions to the candidates:			
1) Answer Q.1 or Q.2 , Q.3 or Q.4 ,Q.5 or Q.6 and Q.7 or Q.8 .			
2) Neat diagrams must be drawn wherever necessary.			
3) Figures to the right side indicate full marks.			
4) Assume Suitable data if necessary			
SECTION I			
Q1)	a)	State conditions to be satisfied for interfacing, by driving & load gate. Draw and explain the interfacing of CMOS driving TTL	[6]
	b)	Minimize the following function using K-map and implement using basic logic gates $f(A,B,C,D) = \sum m(0,1,2,4,8,9,12,13) + d(3,6,7)$	[6]
OR			
Q2)	a)	Convert the following Number into its equivalent Hexadecimal, Decimal & Binary Number (show step-by-step process of conversion): i. $(357.2)_8$ ii. $(458.54)_8$	[6]
	b)	Draw and explain the look ahead carry generator.	[6]
Q3)	a)	Explain the difference between asynchronous and synchronous counter & Convert J- K flip- flop into D-FF. Show the design.	[6]
	b)	Draw an ASM chart of 2 bit up - down counter having a mode control input.	[6]
OR			
Q4)	a)	Draw and explain the behavior of M-S JK flip-flop with waveform.	[6]
	b)	Draw and explain Johnson counter with initial state "1110", from initial state explain all possible states.	[6]
Q5)	a)	Explain the difference between CPLD and FPGA.	[6]
	b)	What is meant by CPLD? Draw & Explain the block diagram of CPLD	[7]
OR			
Q6)	a)	Give the comparison between PROM, PLA and PAL.	[6]
	b)	Design the full adder using PLA.	[7]
Q7)	a)	Explain with example Dataflow and behavioral modeling styles used in VHDL programming.	[6]
	b)	Explain with example 'signal' and 'variable' in VHDL.	[7]
OR			
Q8)	a)	Define entity declaration for AND gate. Also write architecture of AND gate in structural & Data modeling style.	[6]
	b)	What is the difference between behavioral model and structural model in VHDL?	[7]